

**Electricity**  $\rightarrow$  chemical potential  $E \rightarrow$  electric  $E$

static $E$	current of electricity	power
$Q$ charge (C)	$I$ current (A)	$P$ power (W)
$V$ voltage (V)	$R$ resistance ( $\Omega$ )	$E$ electricity (J)

**Symbols**

dry cell	voltmeter	resistor
battery	ammeter	closed switch
wire	bulb	switch open

Types

Circuits

Parts of a circuit

Ammeter

measure of electric current  
— C of charge flowing through every part of the circuit in 1s  
0 resistance

Charge moving produces "friction" which heats up

$\rightarrow$  current = flow in opp direction

produces heating  $\rightarrow$  how much charge is moving  
**Current:** rate of flow of electric charge (C)  
 $I = \frac{Q}{t}$

(current)  
brightness depends on power  
 $P = VI = \frac{W}{s} = I^2 R$   
highest voltage: highest current


Resistance ( $\Omega$ )

- any metal but copper but not more reactive than copper (not insulator)  
 $\rightarrow$  slows  $e^-$  to ensure optimum speed of current  $\rightarrow$   $R_{min}$
  - dependent on material properties and physical dimensions
    - length (long > short)
    - cross sec. area (thin > thick)
    - material
    - temperature (temp  $\uparrow$  res  $\uparrow$ )
      - particular more quicker
      - harder for  $e^-$  to pass through
- (variable resistors)  
**Rheostats**  
used to vary current
- slide control  
 $R = \frac{\rho L}{A}$



Potential difference  
 $R = \frac{V}{I}$

resistivity  
 $R = \frac{\rho L}{A}$

Input transducers

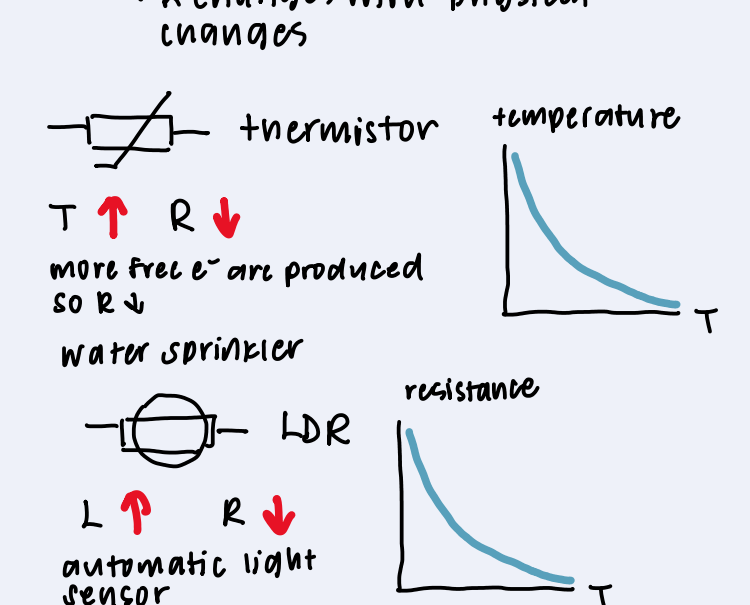

Potential Divider Circuits

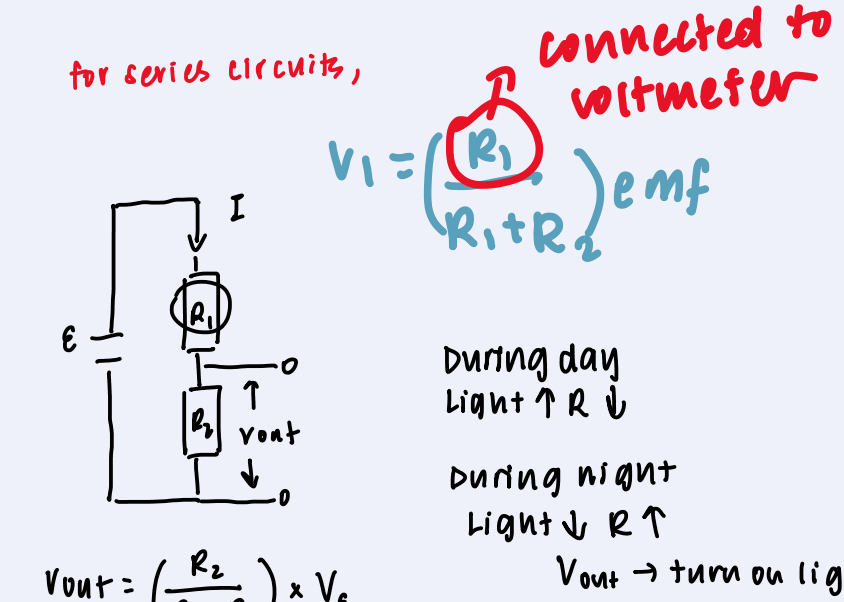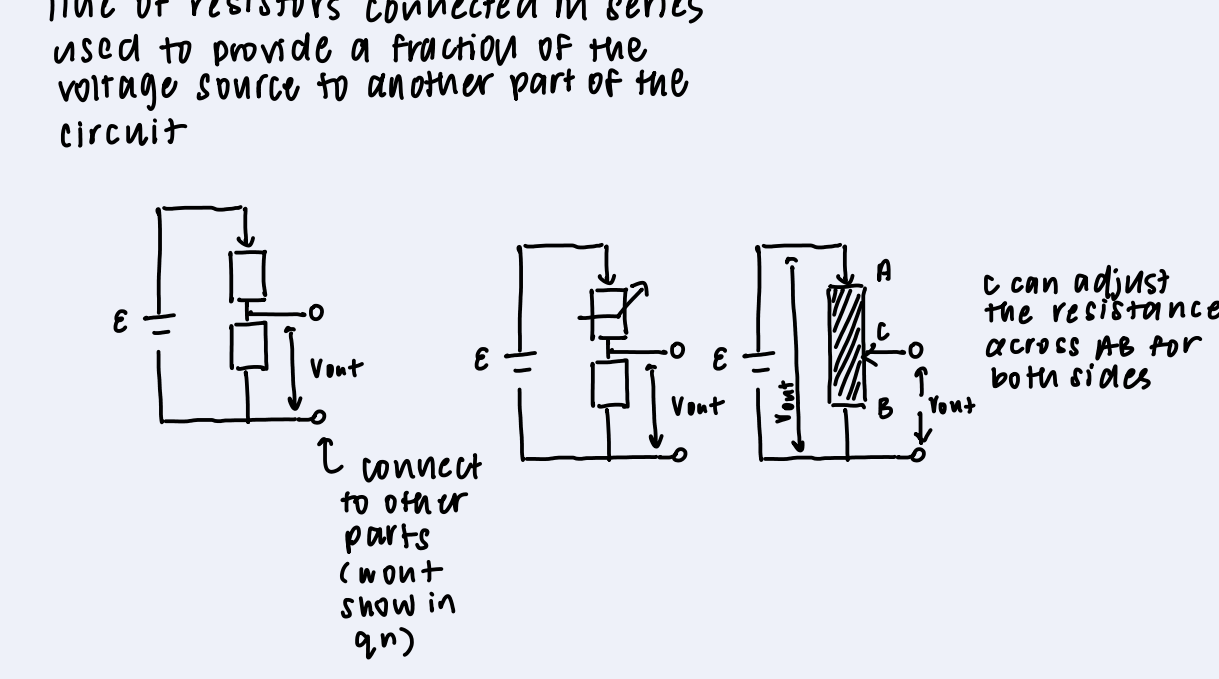

**voltmeter**  
DONT DRAW AT CORNER EG:  
has 0 resistance so current does not flow through  
type of PD (source)  
Electric motive force  
• wd by electric source in driving a unit charge (C) through a circuit connected to the battery  
resistance  
 $V = \frac{W}{Q}$   
EMF / PD (V)

**Copper wire**  
 $e^-$  exists in wire due to delocalised electrons  
 $10^{-18} \text{ s}$

charges moving produces "friction" which heat up...  
chemical  $\rightarrow$  heat  
light  
bulb: another wire

Potential difference ( $V = JC^{-1}$ )

- wd to drive a unit charge through the component
- between 2 points
- can be used for bulbs

Potential

- At a single point in a circuit

OHM'S LAW

current passing through a metallic conductor is directly proportional to the potential difference across it

test  
independent variable  
get 6 sets of values  
plot best fit line  
find slope  
candle stick being investigated

OBEDY  
Ohmic conductors  
- constant res when temp is constant  
 $R = \frac{V}{I}$


DOES NOT OBEY  
non Ohmic conductors  
as long as slope is not a constant

$R \neq \text{slope} \neq \frac{\Delta V}{\Delta I}$   
 $R = \frac{V_0}{I_0} = \frac{V_1}{I_1} = \frac{V_2}{I_2}$

only resistors  
NEVER ALLOWED TO LEAVE SWITCH ON  
in fixed resistor  
Open: carry exp  
Close: take reading

Types of circuits

Series circuits

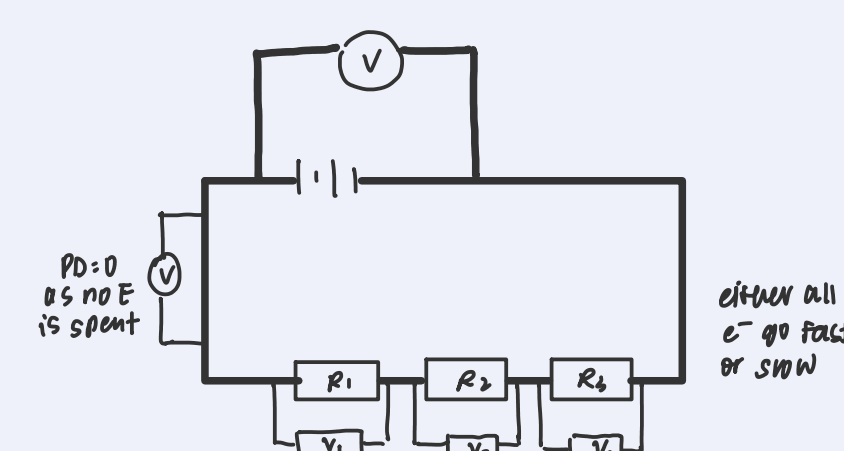

Characteristics

- Only 1 path for current to flow
  - Components are connected 1 after another
- Current in a series circuit is always the same


$R_{\text{eff}} = R_1 + R_2 + R_3$

$I_1 = I_2 = I_3$

$V_1 + V_2 + V_3 = \text{EMF}$

same current but diff res so can't be the same  
split in proportion of resistivity

parallel circuits

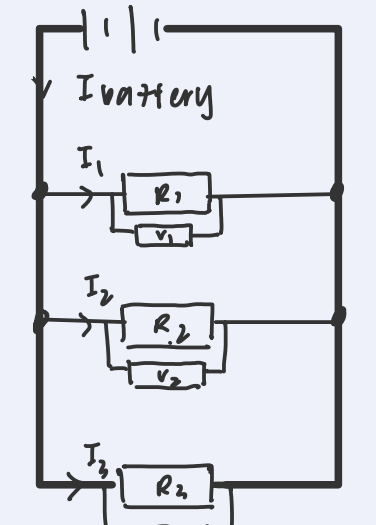

- Components connected in multiple loops
- several paths which electric current can flow through

derived from  $I = \frac{V}{R}$  and  $\Phi$

$R_{\text{eff}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \rightarrow R_{\text{eff}} < R_{\text{min}}$

$I_{\text{battery}} = I_1 + I_2 + I_3$

$V_1 = V_2 = V_3 = \text{EMF}$

Sum of current of each branch is equal to current in main path (current splits)  
All about more resistors: run out of E faster  
PD across whole circuit is equal to the PD across each resistor  
 $V = \frac{W}{Q}$  how much per charge  
 $I = \frac{V}{R}$   
 $V$  is constant  
larger res  $\rightarrow$  less current  
smaller res  $\rightarrow$  more current  
the current "splits" depending on the resistance

Power

$\rightarrow$  how done by appliance

**Electrical power**  
 $P = \frac{W}{t} = \frac{E}{t}$  rate at which E is transformed / changed  
 $P = VI = I^2 R = \frac{V^2}{R}$  usually for power loss  
Power rating  
for bulb, directly proportional to brightness  
240V 2000W  
give me 240V, it'll work at 2000W and give a brightness of  
when optimal PD is used, bulb will dissipate E at the rate of  $V$  and shine at "normal brightness"

5 bill in kWh  
kilowatt hr